

Basic Electrical Engineering (TEE 101)

*Lecture 4: Analysis of Voltage,
current sources and Resistances
in series and parallel*

Content

**This lecture covers
the analysis of :**

**Voltages sources in
series**

**Current sources in
parallel**

**Resistances in
Series and Parallel**

Voltage Sources Connected in Series


Voltage sources when connected in series either aid each other or oppose each other.

It depends on the direction of the polarities of the voltage sources, Or, we can say on the direction of the electric field

If the polarities of two voltage sources (V_1 and V_2) connected in series are same, then the total voltage (V) is the sum of two voltages (V_1 and V_2), i.e. $V = V_1 + V_2$

If the polarities of both voltage sources is opposite to each other, then the net voltage is the difference of the two voltages (i.e. $V = V_1 - V_2$)

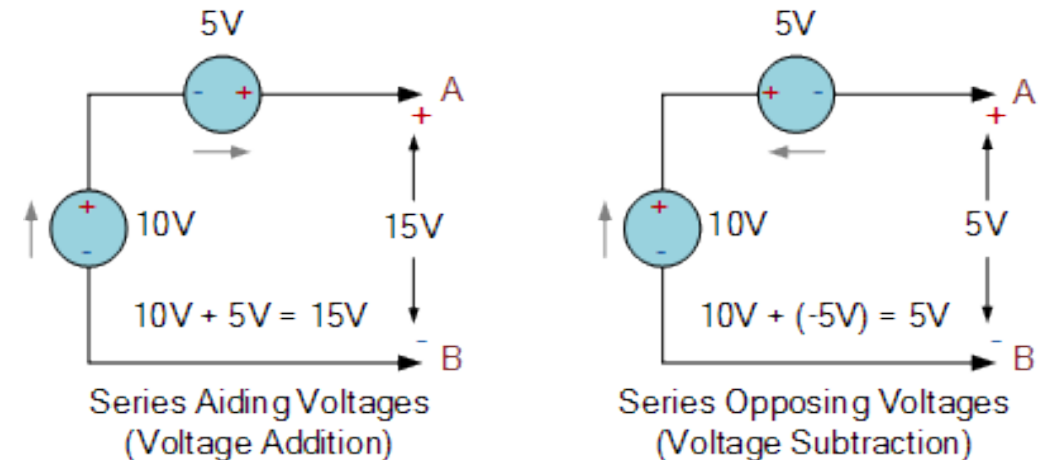This is illustrated in the diagrams below:




Current Source in Parallel

Just like voltage sources, ideal current sources can also be connected together to increase (or decrease) the available current.


When two or more current sources connected in parallel to each other, the currents are added.

When current sources are connected anti parallel, then the net current is algebraic sum of all currents

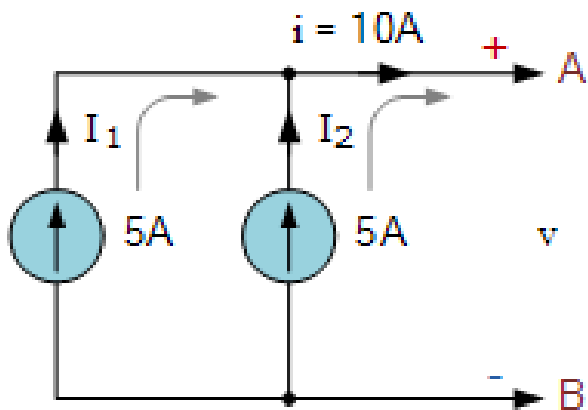
Connecting two or more current sources in parallel is equivalent to one current source whose total current output is given as the algebraic addition of the individual current source.




current sources in same direction

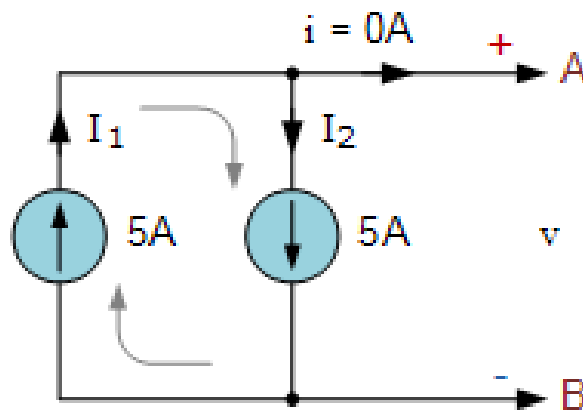

current sources in opposite direction

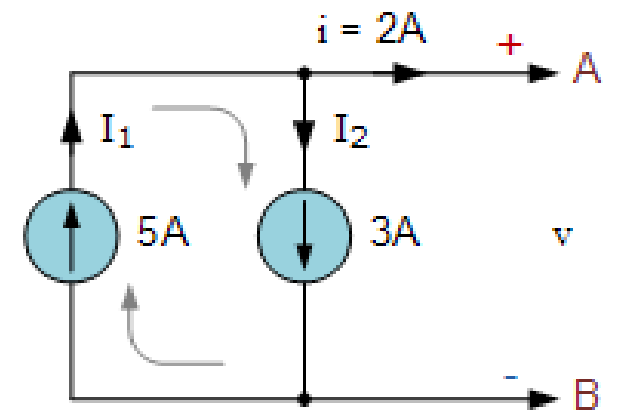


Resistances in Series

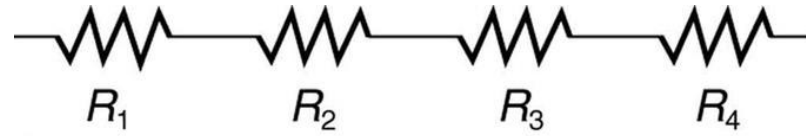

The total resistance in the circuit with resistors connected in series is equal to the sum of the individual resistances.

Consider a circuit as shown below. According to Ohm's law, the voltage drop, V , across a resistor when a current flows through it is calculated by using the equation $V=IR$,

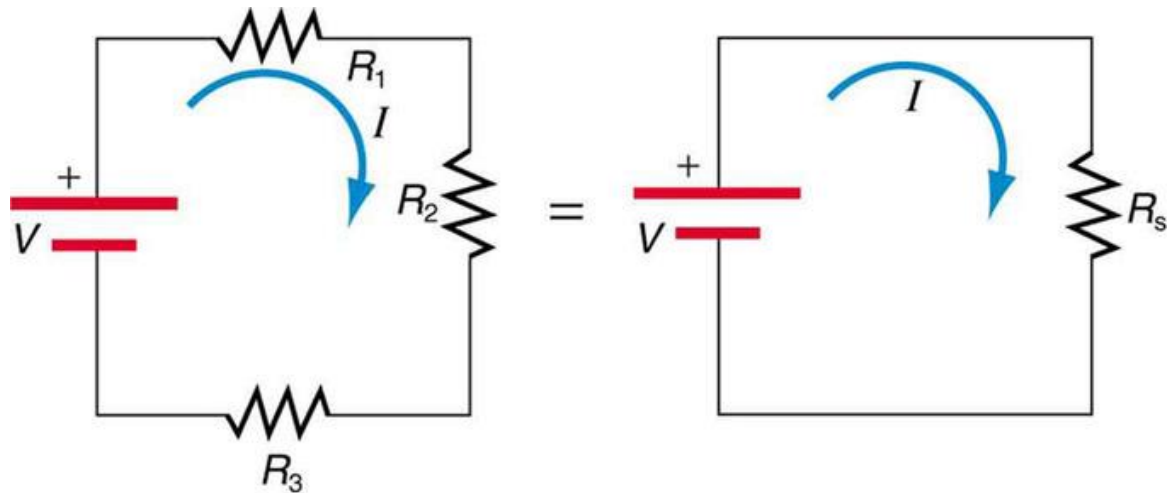- *where V is in Volts, I is current in Amps (A) and R_s is the resistance in ohms (Ω).*



So the voltage drop across R_1 is: $V_1=IR_1$, across R_2 is $V_2=IR_2$, and across R_3 is $V_3=IR_3$.

The sum of the voltages would equal: $V=V_1+V_2+V_3$, based on the conservation of energy and charge.

If we substitute the values for individual voltages, we get: $V=IR_1+IR_2+IR_3$

- Or, $V=I(R_1+R_2+R_3)$
- Or, $V/I = R_1+R_2+R_3$
- $V/I = R_s$, Hence: $R_s = R_1+R_2+R_3$


This implies that the total resistance in a series is equal to the sum of the individual resistances.

Therefore, for every circuit with N number of resistors connected in series:

$$R_s=R_1+R_2+R_3+...+R_N$$

Resistances in Parallel

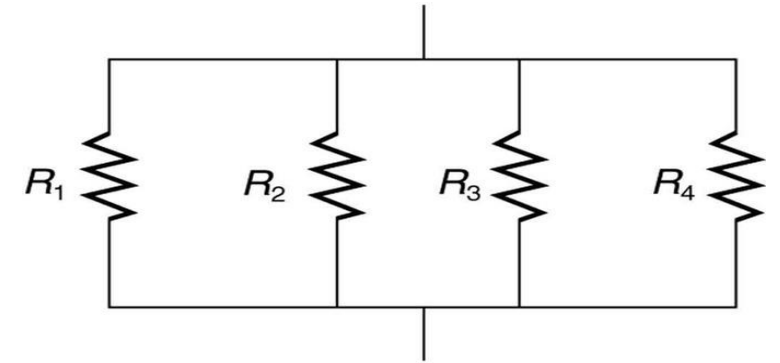
Resistors are in parallel when each resistor is connected directly to the voltage source by connecting wires having negligible resistance.



Consider a circuit as shown below. According to Ohm's law, the currents flowing through the individual resistors are

$$I_1 = \frac{V}{R_1} \quad I_2 = \frac{V}{R_2} \quad I_3 = \frac{V}{R_3}$$

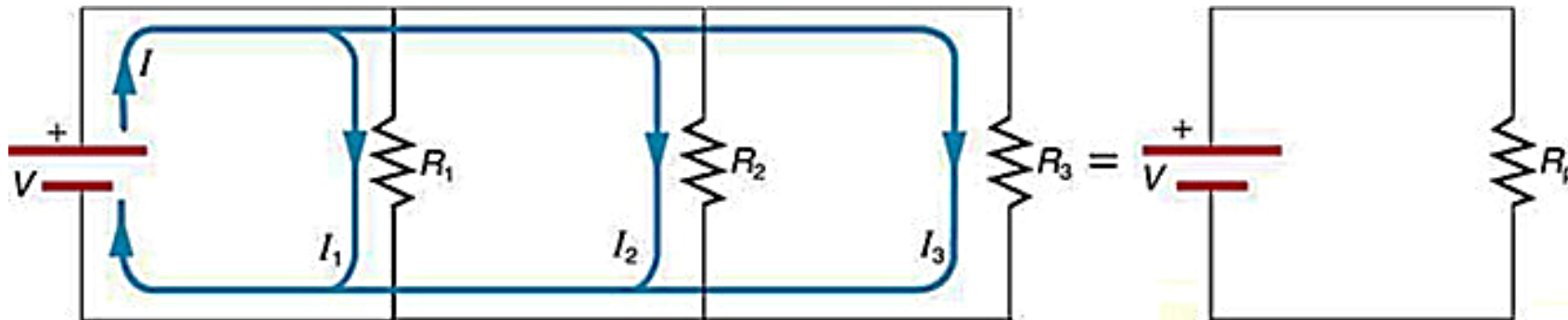- *where V is in Volts (V), I is current in amps (A) and R_p is the resistance in ohms (Ω).*



Conservation of charge implies that the total current is the sum of these currents:

$$I = I_1 + I_2 + I_3.$$

Substituting the expressions for individual currents gives:

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\text{Or, } I = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\text{Or, } \frac{I}{V} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$



$$\text{Or, } \frac{1}{R_P} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$



$$\text{Where, } R_P = \frac{V}{I}$$

This implies that the total resistance in a parallel circuit is equal to the sum of the inverse of each individual resistances.

Therefore, for every circuit with “N” number of resistors connected in parallel,
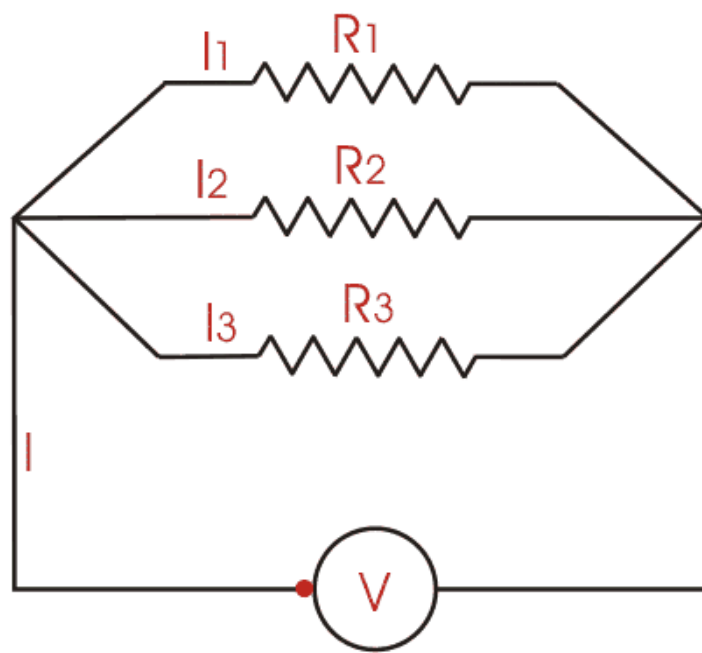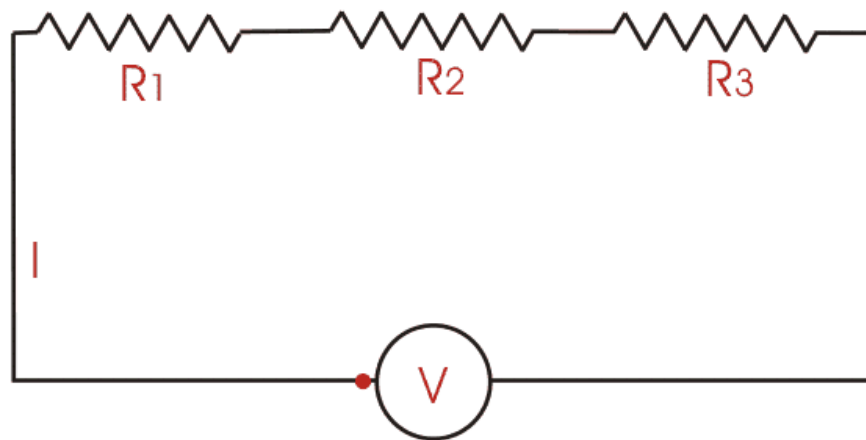
$$\frac{1}{R_P} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N} \right)$$



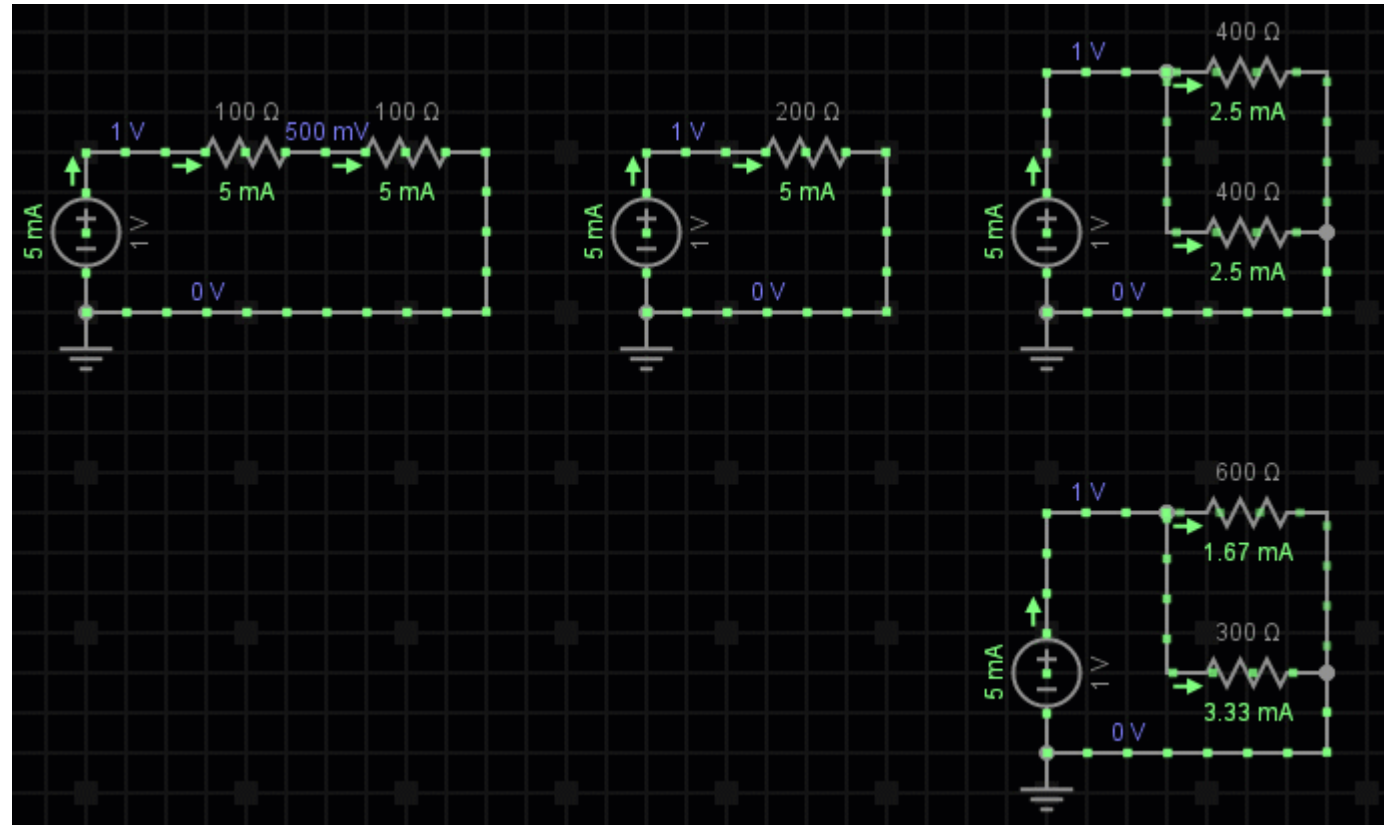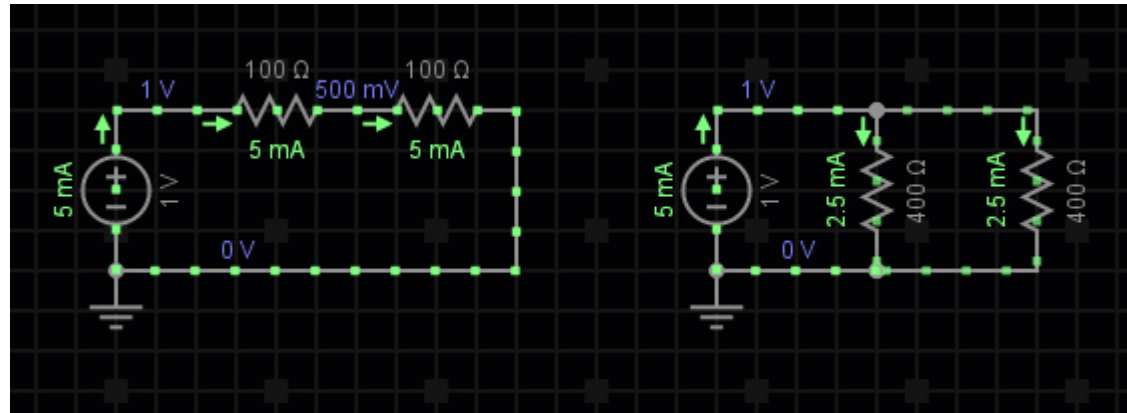

Thank You