

Basic Electrical Engineering (TEE 101)

Lecture 9: Numerical Practice on Mesh Analysis

Content


This lecture covers the numerical practice on Mesh Analysis for the:

Circuit with two meshes

Super mesh Case

Case – 1: Circuit with 2 meshes and voltage sources

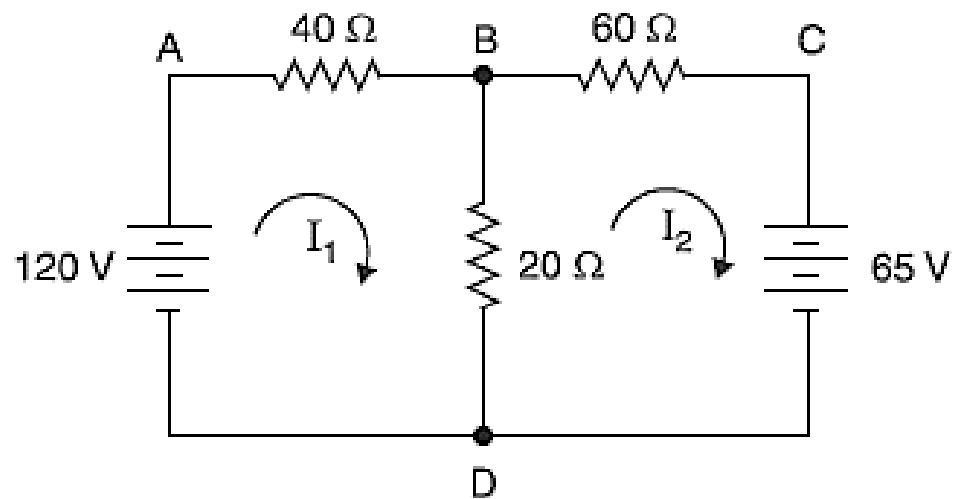In the network shown in Figure below, find the magnitude of each branch current by mesh current method.



Step 1 :- Identify the number of meshes.

Step 2 :- Take current in each branch of the network and assume their direction. You can assume any direction of branch current in bilateral circuits.

Step 3 :- Now, assume the current in each mesh. The direction of mesh currents can be taken either clockwise or anti-clockwise.


In this circuit, there are 02 meshes.
Hence, there will be 02 mesh equations in this problem.

Mark these mesh currents.
Let these currents are

I_1 and I_2

and are circulating in
clockwise direction

Now, let's draw the circuit
diagram

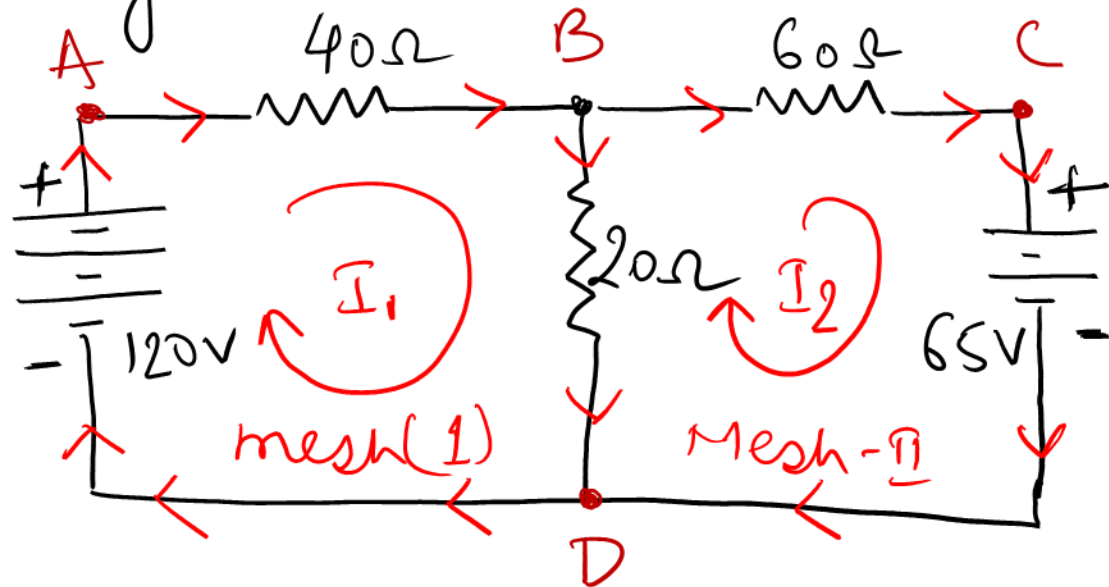

The KVL equation of mesh-1
is :

$$120 + (-I_1 \times 40) - (I_1 - I_2) \times 20 = 0$$

$$120 - 40I_1 - 20I_1 + 20I_2 = 0$$

$$-60I_1 + 20I_2 = -120$$

$$3I_1 - I_2 = 6$$

Similarly, apply KVL in mesh-2
we get :

$$-60 \times I_2 - 65 - (I_2 - I_1) \times 20 = 0$$

$$-60I_2 - 65 - 20I_2 + 20I_1 = 0$$

$$20I_1 - 80I_2 = 65$$

$$4I_1 - 16I_2 = 13 \quad \text{--- (2)}$$

We can solve eqⁿ (1) and (2) to calculate the mesh currents I_1 and I_2 .

$$[3I_1 - I_2 = 6] \times 16$$

$$[4I_1 - 16I_2 = 13] \times 1$$

$$48I_1 - 16I_2 = 96$$

$$4I_1 - 16I_2 = 13$$

$$\begin{array}{r} 48I_1 - 16I_2 = 96 \\ - \quad 4I_1 - 16I_2 = 13 \\ \hline 44I_1 = 83 \end{array}$$

$$I_1 = \frac{83}{44} = 1.886 \text{ A} \quad \text{--- (3)}$$

The value of I_2 can be calculated using the value of I_1 in either eqⁿ (1) or (2). So,

$$4 \times \left(\frac{83}{44} \right) - 16I_2 = 13$$


$$I_2 = -0.341 \text{ A} \quad \text{--- (4)}$$

The current through branch BD is

$$\begin{aligned} I_1 - I_2 &= 1.886 - (-0.341) \\ &= 2.227 \text{ A} \quad \text{--- (5)} \end{aligned}$$

Case -3: Super Mesh Case

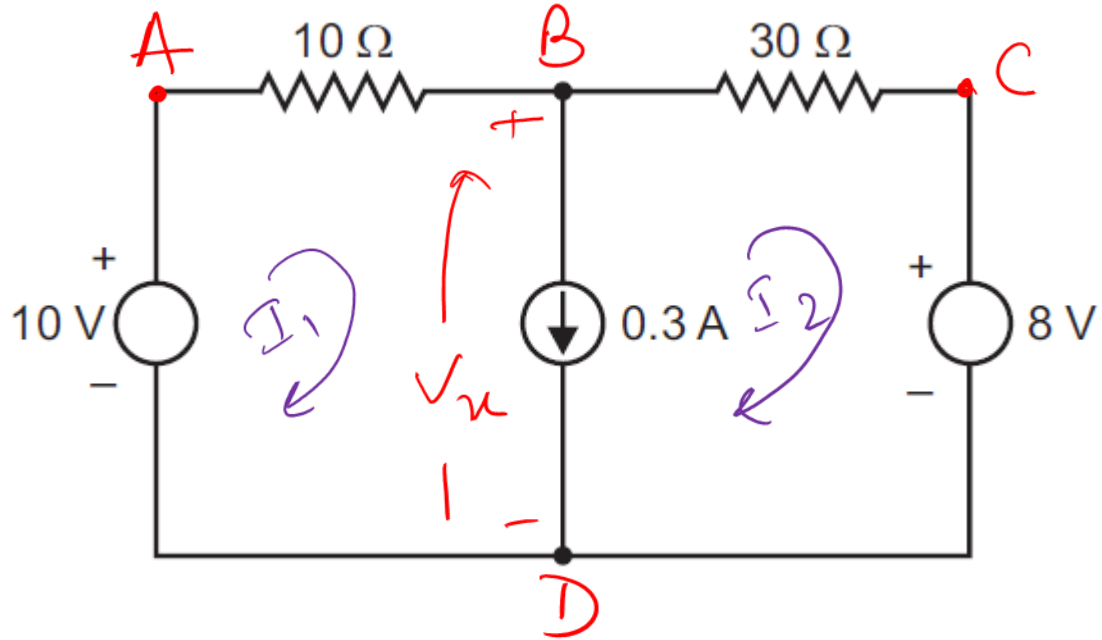Use mesh current method to determine currents through each of the resistance in the circuit shown in Figure below:



A super mesh take place when a current source is contained between two essential meshes. The circuit is first treated as if the current source is not there. This leads to one equation that incorporates two mesh currents.

Let us assume a voltage across the current source, which is (for example) V_x
Now apply KVL

$$10 - 10I_1 - V_x = 0 \quad \text{--- (1)}$$

and

$$-30I_2 - 8 + V_x = 0 \quad \text{--- (2)}$$

add eqⁿ (1) and (2)

$$(10 - 10I_1 - V_x) + (-30I_2 - 8 + V_x) = 0$$

$$\text{or, } 10 - 8 - 10I_1 - 30I_2 = 0$$

$$\text{or, } -10I_1 - 30I_2 = -2$$

$$\text{or, } \boxed{5I_1 + 15I_2 = 1} \quad \text{--- (3)}$$

Now; The current in the current source can be written as:

$$\boxed{I_1 - I_2 = 0.3} \quad \text{--- (4)}$$

Now, we can solve eqⁿ (3) and (4) to determine the values of I_1 and I_2 .

$$[5I_1 + 15I_2 = 1] \times 1$$

$$[I_1 - I_2 = 0.3] \times 5$$

$$\cancel{5I_1} + 15I_2 = 1$$

$$\cancel{5I_1} - 5I_2 = 1.5$$

$$20I_2 = -0.5$$

$$I_2 = \frac{-0.5}{20} = -0.025 \text{ A}$$

Substitute this value of I_2 in any eqⁿ (i.e either eqⁿ ③ or eqⁿ ④) we get

$$I_1 - (-0.025) = 0.3$$

$$\text{or, } I_1 + 0.025 = 0.3$$

$$I_1 = 0.3 - 0.025$$

$$I_1 = 0.275 \text{ A}$$

$$I_2 = -0.025 \text{ A}$$

\Rightarrow Ans

The negative sign of I_2

Indicates that the actual direction of flow of this current is opposite to that we assumed.

i.e the current is flowing from $D \rightarrow C \rightarrow B$ and not from $B \rightarrow C \rightarrow D$ as assumed



Thank You