

Basic Electrical Engineering (TEE 101)

Lecture 43: Practical Transformer on Load – Part 2

Content


This lecture covers:

**Phasor Diagram of Practical
Transformer for Inductive
Load
(i.e. Lagging Power Factor)**

**Phasor Diagram of Practical
Transformer for Resistive
Load
(i.e. Unity Power Factor)**

**Phasor Diagram of Practical
Transformer for Capacitive
Load
(i.e. Leading Power Factor)**

Important Parameters

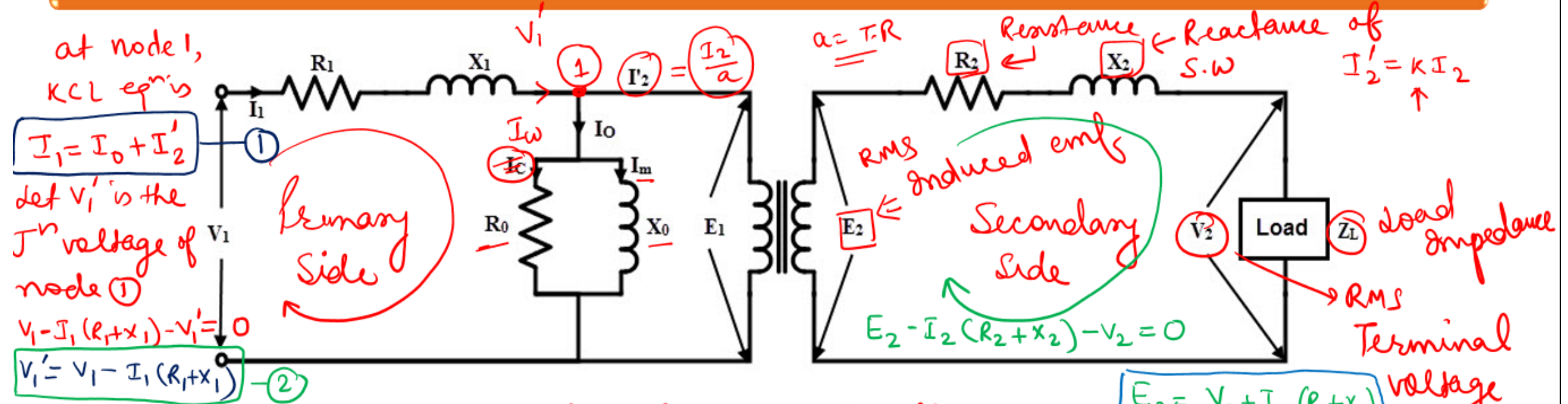

I_w = RMS value of real component of I_0

I_m = RMS value of the magnetising component of I_0

V_1 = RMS value of the input voltage (V_1)

I_1 = RMS value of the full load primary current

I_0 = RMS value of the NO-load primary current

I_2' = RMS value of the full primary counter current

E_1 = " " " " Induced emf in the primary winding

R_1 & $X_1 \Rightarrow$ winding Resistance and Reactance of the Primary "

R_0 & $X_0 \Rightarrow$ Core parameters (under NO-load condition)

Phasor Diagram of Practical Transformer for Inductive Load

$Z_L \in \text{Inductive}$

NOT Pure Inductor



In an R-L load
the current
lags the voltage
by ϕ

from the emf eqⁿ concept

$$\begin{cases} \phi = \phi_m \sin \theta \\ e_1 = E_m \sin(\theta - 90^\circ) \\ e_2 = E_m \sin(\theta - 90^\circ) \end{cases}$$

$\therefore Z_L = \text{Inductive}$
hence, I_2 lags V_2 by ϕ_2

$I_1 x_1$ leads
 I_1 by 90°

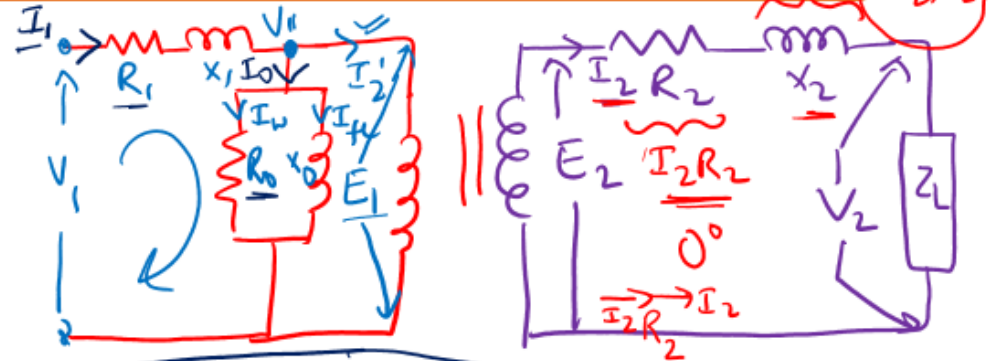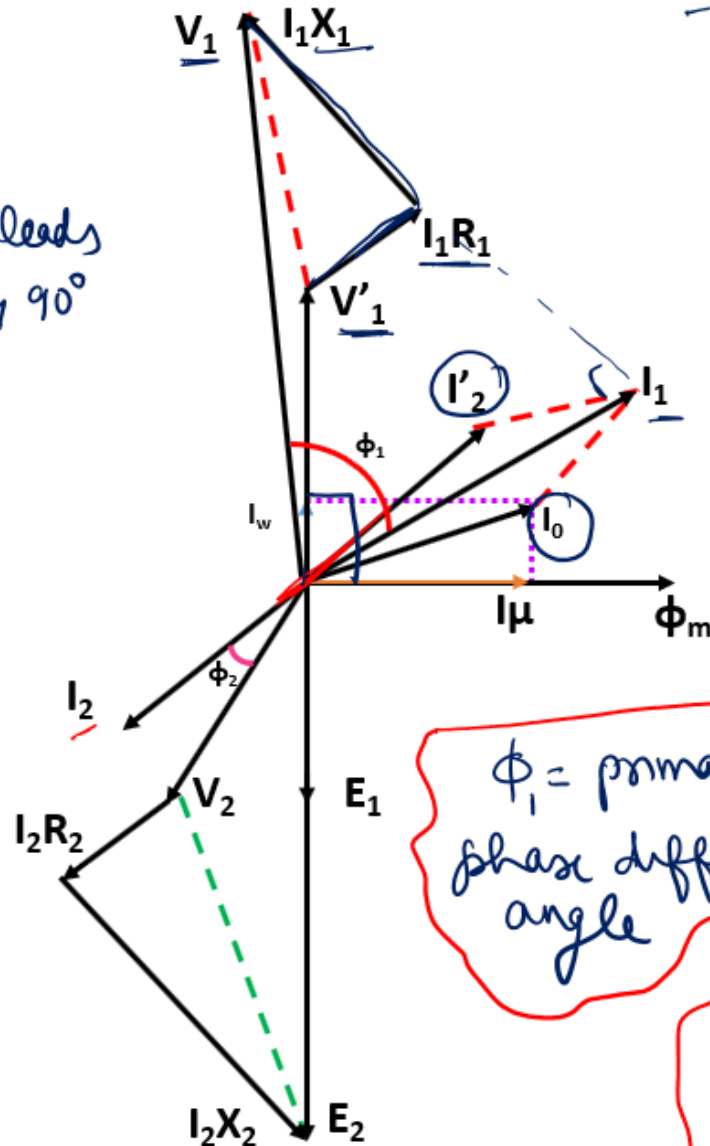

$$\begin{aligned} V_1 &= I_1 R_1 - I_1 x_1 - V'_1 = 0 \\ V'_1 &= V_1 - I_1 (R_1 + X_1) \end{aligned}$$

cause of

$$V_1 = V'_1 + I_1 R_1 + I_1 x_1$$

$E_1 \propto V'_1$

as per Lenz's law, E_1 opposes V'_1

$I_0 = \text{no load current}$

$$I_0 = I_w + I_\mu$$

$\phi_1 = \text{primary phase difference angle}$

voltage across
 R_0 & X_0 is V'_1
 I_w & V'_1 are in phase
 I_μ lags V'_1 by $\pi/2$ rad


$$\begin{aligned} E_2 &= V_2 + I_2 R_2 + I_2 X_2 \\ &= V_2 + I_2 (R_2 + X_2) \end{aligned}$$

Phasor Diagram of Practical Transformer for Resistive Load

This is for the unity p.f

$$Z_L = R$$

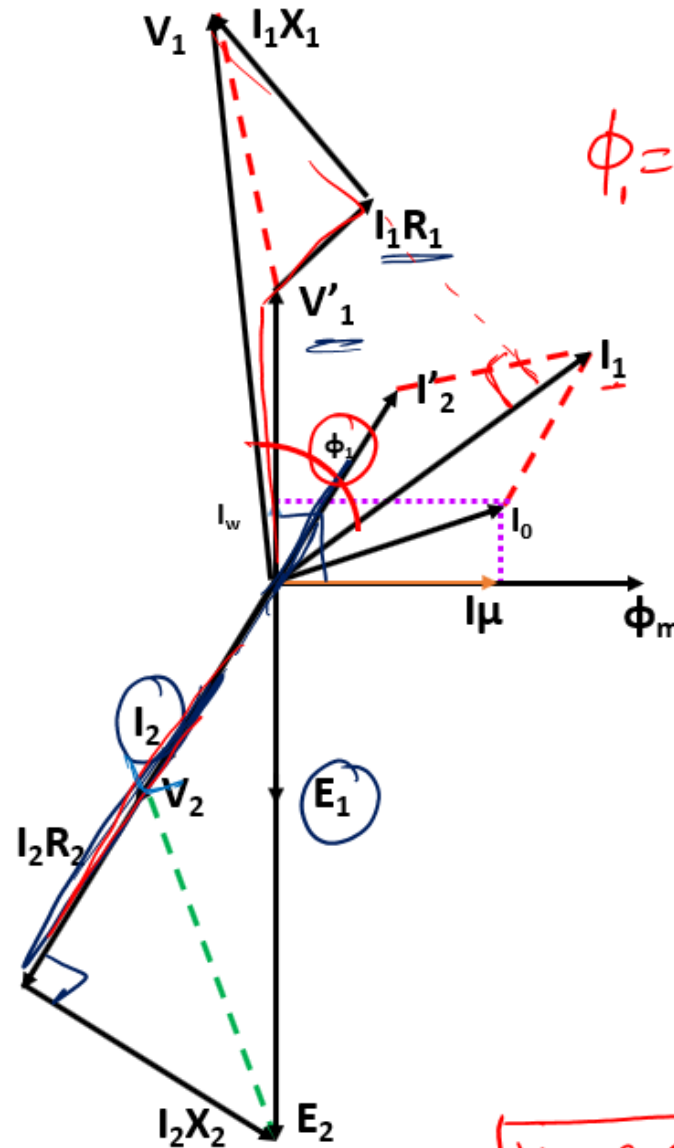In a resistance the voltage & current are in same phase.




ϕ_1 = primary winding phase diff. b/w V_1 & I_1



$I_2 R_2$ & I_2 are in phase

$\frac{I_2 X_2}{90^\circ}$ leads I_2 by

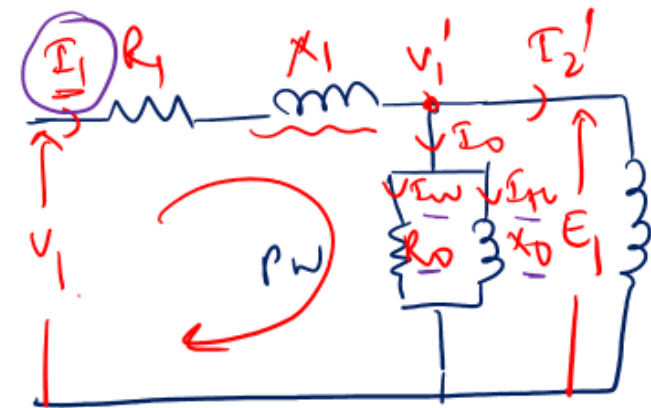

$$V_1 = I_1 R_1 + I_1 X_1 + V_1'$$

$I_1 X_1$ leads I_1 by 90°

Phasor Diagram of Practical Transformer for Capacitive Load

$$Z_L = R - jC \text{ (re capacitance)}$$

In this case,


I_2 (full load secondary current)

leads

V_2 (full load terminal voltage of secondary)

by angle ϕ_2

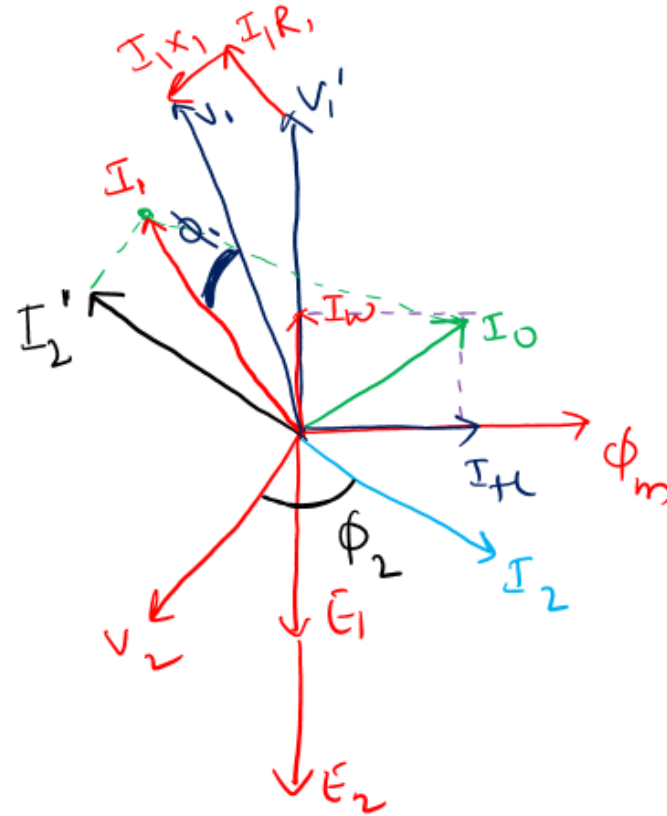$\phi_2 =$ phase difference angle between V_2 and I_2 for capacitive load



Phasor diagram of transformer for a capacitive load i.e. for leading p.f (power factor)

Thank You