

Basic Electrical Engineering (TEE 101)

Lecture 41: Transformer on NO - Load

Content

This lecture covers:

Transformer on NO - Load

**Phasor Diagram of
Transformer on NO - Load**

Numerical Examples

Introduction

A transformer is said to be on *no-load* if its secondary side is open and primary is connected to a sinusoidal alternating voltage V_1 .

Under No-Load condition, a low (about 2% to 5% of the rated primary current) current flows through the primary winding. It is denoted as I_0

This primary input current (I_0) under no-load conditions is responsible for :

(i) *Iron losses in the core (i.e., hysteresis loss and eddy current loss).*

(ii) *A very small amount of copper losses in primary (there being no copper loss in the secondary as it is open).*

No-load current (I_0) consists of two components I_w and I_μ or I_m .

I_w is the wattful/active component and it supplies for the core loss in the transformer.

I_μ or I_m is the wattless/reactive component and it sets up flux in the core

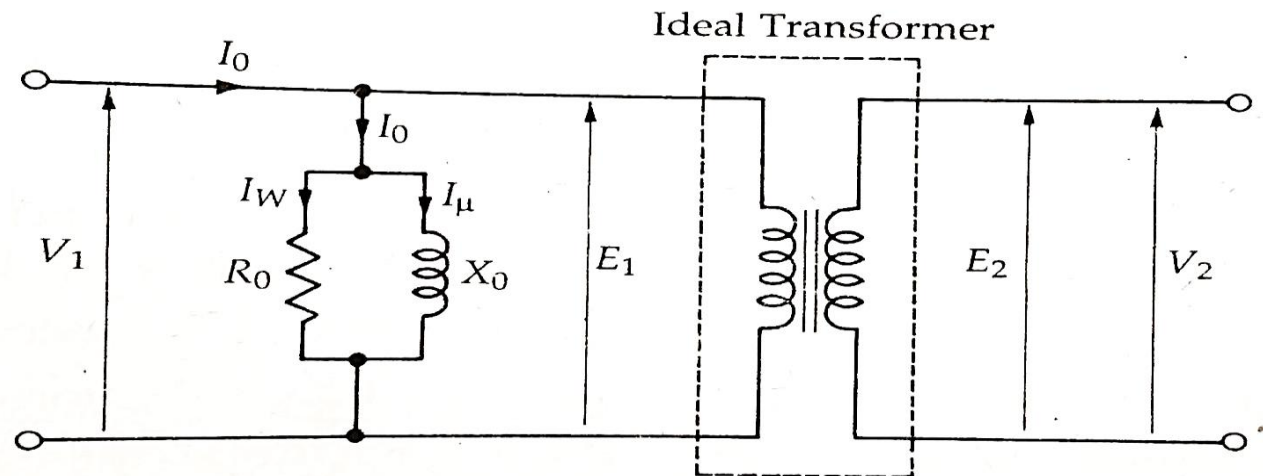


Figure 1: NO-LOAD EQUIVALENT CIRCUIT OF A TRANSFORMER

Phasor Diagram

Figure 1 represents the phasor diagram of transformer under NO - Load condition.

(i) **Active component I_w .** This component is in *phase with V_1* and mainly supplies the iron loss plus small quantity of primary copper loss. It is the wattful or active component of the primary no-load current. $I_w = I_0 \cos \phi_0 \dots(i)$

(ii) **Reactive component I_μ or I_m** This component lags V_1 by 90° and its function is to *sustain the alternating flux in the core*. It is *wattless component of the primary no-load current*. It is also known as magnetizing component. $I_m = I_0 \sin \phi_0 \dots(ii)$

Also
$$I_0 = \sqrt{I_w^2 + I_m^2} \dots(iii)$$

Thus I_0 is not at 90° behind V_1 , but lags it by an angle $\phi_0 < 90^\circ$.

No-load power input, $P_0 = V_1 I_0 \cos \phi_0$

where $\cos \phi_0$ = primary power factor under no-load conditions.

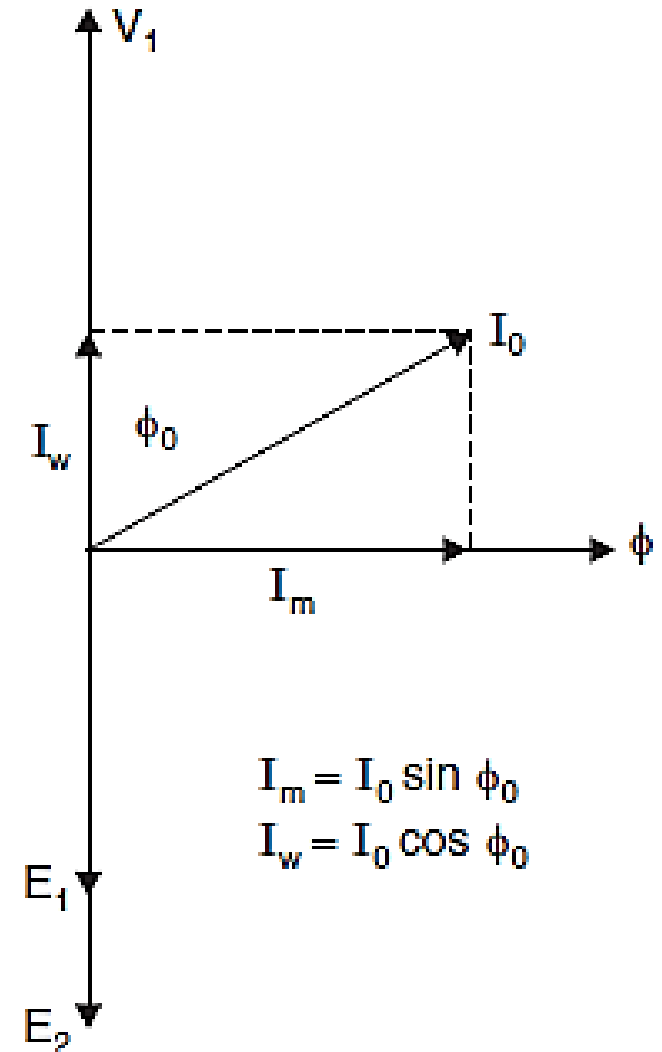


Figure 2: No-load vector diagram

Example 1. A 3300/300 V single-phase transformer gives 0.6 A and 60 W as ammeter and wattmeter readings when supply is given to the low voltage winding and high voltage winding is kept open, find :

(i) Power factor of no-load current. (ii) Magnetizing component. (iii) Iron loss component.

Solution. No-load losses, $P_0 = 60 \text{ W}$

No-load current, $I_0 = 0.6 \text{ A}$

(i) $P_0 = VI_0 \cos \phi_0$

$\therefore 60 = 300 \times 0.6 \times \cos \phi_0$

$$\cos \phi_0 = \frac{60}{300 \times 0.6} = 0.33 \text{ (lagging)}$$

Hence, **power factor of no-load current = 0.33. (Ans.)**

(ii) Magnetising component, $I_m = I_0 \sin \phi_0 = 0.6 \sqrt{1 - \cos^2 \phi_0} = 0.6 \sqrt{1 - (0.33)^2} = 0.566 \text{ A}$

$\therefore I_m = \mathbf{0.566 \text{ A. (Ans.)}}$

(iii) Iron loss component, $I_w = I_0 \cos \phi_0 = 0.6 \times 0.33 = \mathbf{0.198 \text{ A. (Ans.)}}$

$$I_w = \sqrt{I_0^2 - I_m^2} = \sqrt{(0.6)^2 - (0.566)^2} = 0.198 \text{ A}].$$

Example 2. Find (i) active and reactive components of no-load current ; and (ii) no-load current of a 440/220 V single-phase transformer if the power input on no-load to the high voltage winding is 80 W and power factor of no-load current is 0.3 lagging.

Solution. Primary, $E_1 = 440 \text{ V}$
 Secondary, $E_2 = 220 \text{ V}$
 Power factor, $\cos \phi_0 = 0.3$ (lagging)
 No-load losses, $P_0 = 80 \text{ W}$
 (i) **Active component** (or *wattful component*),

$$I_w = (I_0 \cos \phi_0) = \frac{P_0}{V_1} = \frac{80}{440} = \mathbf{0.182 \text{ A. (Ans.)}}$$

$$\cos \phi_0 = 0.3 ; \phi_0 = \cos^{-1} (0.3) = 72.54^\circ$$

$$\therefore \tan \phi_0 = 3.18$$

Reactive component (or *magnetizing components*)

$$I_m = I_w \tan \phi_0 = 0.182 \times 3.18 = \mathbf{0.578 \text{ A. (Ans.)}}$$

$$(ii) \quad I_w = I_0 \cos \phi_0$$

$$\therefore I_0 = \frac{I_w}{\cos \phi_0} = \frac{0.182}{0.3} = \mathbf{0.606. (Ans.)}$$

$$[or \quad I_0 = \sqrt{I_w^2 + I_m^2} = \sqrt{(0.182)^2 + (0.578)^2} = 0.606 \text{ A}].$$

Example 3. A 3300/220 V, 30 kVA, single-phase transformer takes a no-load current of 1.5 A when the low voltage winding is kept open. The iron loss component is equal to 0.4 A find :

(i) No-load input power.

(ii) Magnetizing component and power factor of no-load current.

Solution. Rating of transformer = 30 kVA

Primary, $E_1 = 3300 \text{ V}$

Secondary, $E_2 = 220 \text{ V}$

No-load current, $I_0 = 1.5 \text{ A}$

Iron loss component, $I_m = 0.4 \text{ A}$

(i) **No-load input power,**

$$\begin{aligned} P_0 &= V_1 I_0 \cos \phi_0 = V_1 I_w & (\because I_w = I_0 \cos \phi_0) \\ &= 3300 \times 0.4 = \mathbf{1320 \text{ W.}} \quad (\text{Ans.}) \end{aligned}$$

(ii) **Magnetising component,**

$$I_m = \sqrt{I_0^2 - I_w^2} = \sqrt{1.5^2 - 0.4^2} = \mathbf{1.44 \text{ A.}} \quad (\text{Ans.})$$

No-load power factor,

$$\cos \phi_0 = \frac{I_w}{I_0} = \frac{0.4}{1.5} = \mathbf{0.267.} \quad (\text{Ans.})$$

Thank You